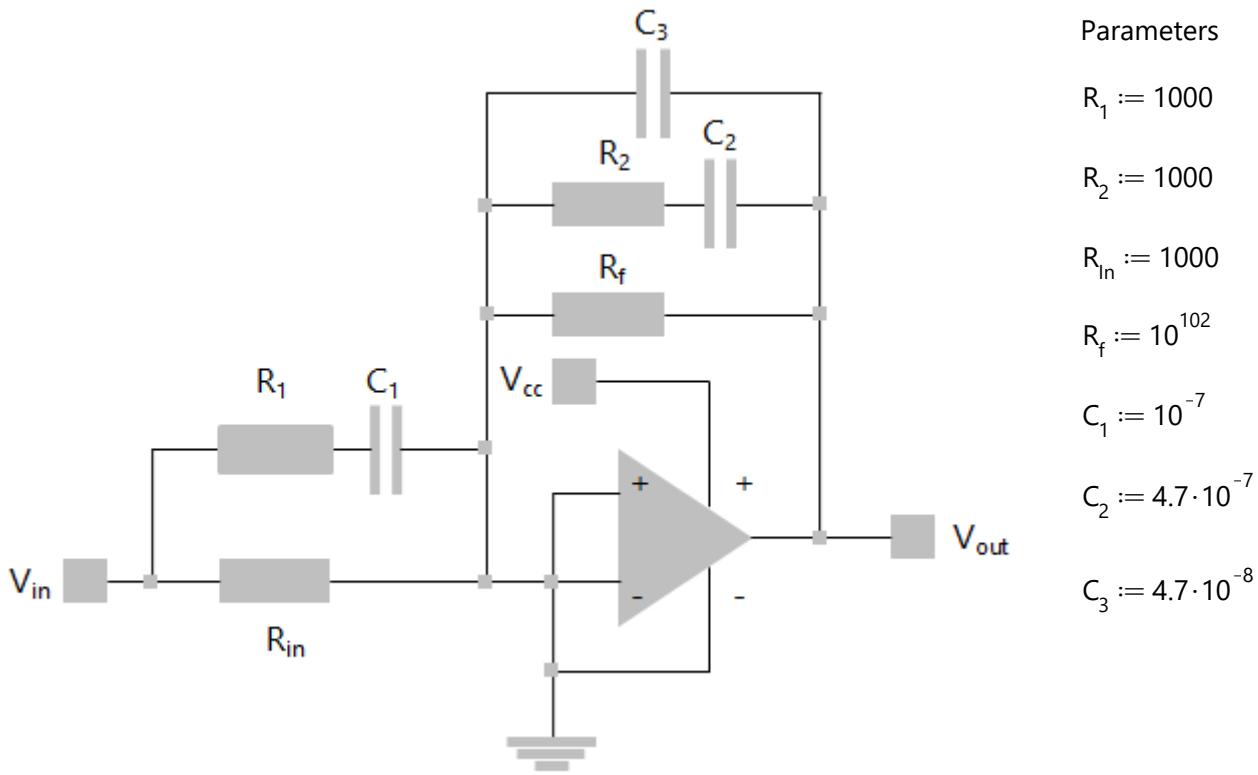


Amplifier Gain

In this application, we will plot the gain of this amplifier circuit, for both the ideal and non-ideal response.



Amplifier bandwidth factors

$$GBP := 10^6$$

$$LPF := 300$$

Support function

$$\Pi := (Z_1, Z_2) \quad \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$

Derivation of transfer functions

$$Z_1 := R_1 + \frac{1}{s \cdot C_1} = 1.00 \times 10^3 + \frac{1.00 \times 10^7}{s}$$

$$Z_2 := R_2 + \frac{1}{s \cdot C_2} = 1.00 \times 10^3 + \frac{2.13 \times 10^6}{s}$$

$$Z_{in} := \text{simplify}(\Pi(R_{in}, Z_1)) = \frac{5.00 \times 10^6 + 5.00 \times 10^2 \cdot s}{5.00 \times 10^3 + s}$$

$$Z_{fb} := \left| R_f \right| \left| \left(Z_2, \frac{1}{s \cdot C_3} \right) \right|$$

Ideal amplifier gain

$$G_{EAideal} := \text{factor} \left(\frac{Z_{fb}}{Z_{in}} \right)$$

$$G_{EAideal} = \frac{(4.26 \times 10^4 \cdot s + 9.05 \times 10^7) \cdot (5.00 \times 10^3 + s)}{(s + 2.34 \times 10^4) \cdot (s + 1.93 \times 10^{-96}) \cdot (1.00 \times 10^4 + s)}$$

Finite open loop gain

$$A_{vo} := \frac{GBP}{LPF} \cdot \frac{1}{\left(1 + \frac{s}{2 \cdot \pi \cdot LPF} \right) \cdot \left(1 + \frac{s}{2 \cdot \pi \cdot GBP} \right)}$$

$$A_{vo} = \frac{3.33 \times 10^3}{(1 + 5.31 \times 10^{-4} \cdot s) \cdot (1 + 1.59 \times 10^{-7} \cdot s)}$$

Non-deal op-amp effect

$$\beta := \frac{1}{1 + G_{EAideal}}$$

$$fnormal(\beta) = \frac{s \cdot (s + 2.34 \times 10^4) \cdot (1.00 \times 10^4 + s)}{s^3 + 7.60 \times 10^4 \cdot s^2 + 5.37 \times 10^8 \cdot s + 4.53 \times 10^{11}}$$

Non-ideal error amplifier gain

$$G_{EA} := \text{simplify} \left(G_{EAideal} \cdot \frac{1}{1 + 1 / (A_{vo} \cdot \beta)} \right)$$

$$G_{EA} = \frac{1.79 \times 10^{25} + 1.68 \times 10^{18} \cdot s^2 + 1.20 \times 10^{22} \cdot s}{5.36 \times 10^{21} + s^5 + 6.36 \times 10^6 \cdot s^4 + 4.00 \times 10^{13} \cdot s^3 + 1.32 \times 10^{18} \cdot s^2 + 9.25 \times 10^{21} \cdot s}$$

Plot the frequency response

$$\text{sys1} := \text{DynamicSystems:-TransferFunction}(G_{EA})$$

$$\text{sys2} := \text{DynamicSystems:-TransferFunction}(G_{EAideal})$$

$$p1 := \text{DynamicSystems:-PhasePlot}(\text{sys1}, \text{range} = 10 .. 10^5, \text{hertz} = \text{true}, \text{legend} = \text{"Non Ideal"})$$

$$p2 := \text{DynamicSystems:-PhasePlot}(\text{sys2}, \text{range} = 10 .. 10^5, \text{hertz} = \text{true}, \text{legend} = \text{"Ideal"}, \text{color} = \text{black})$$

```
plots:-display( p1, p2, size = [ 800, 400 ], labelfont = [ Arial ],
axesfont = [ Arial ], legendstyle = [ location = bottom, font = [ Arial ] ],
axes = boxed, gridlines ) =
```

