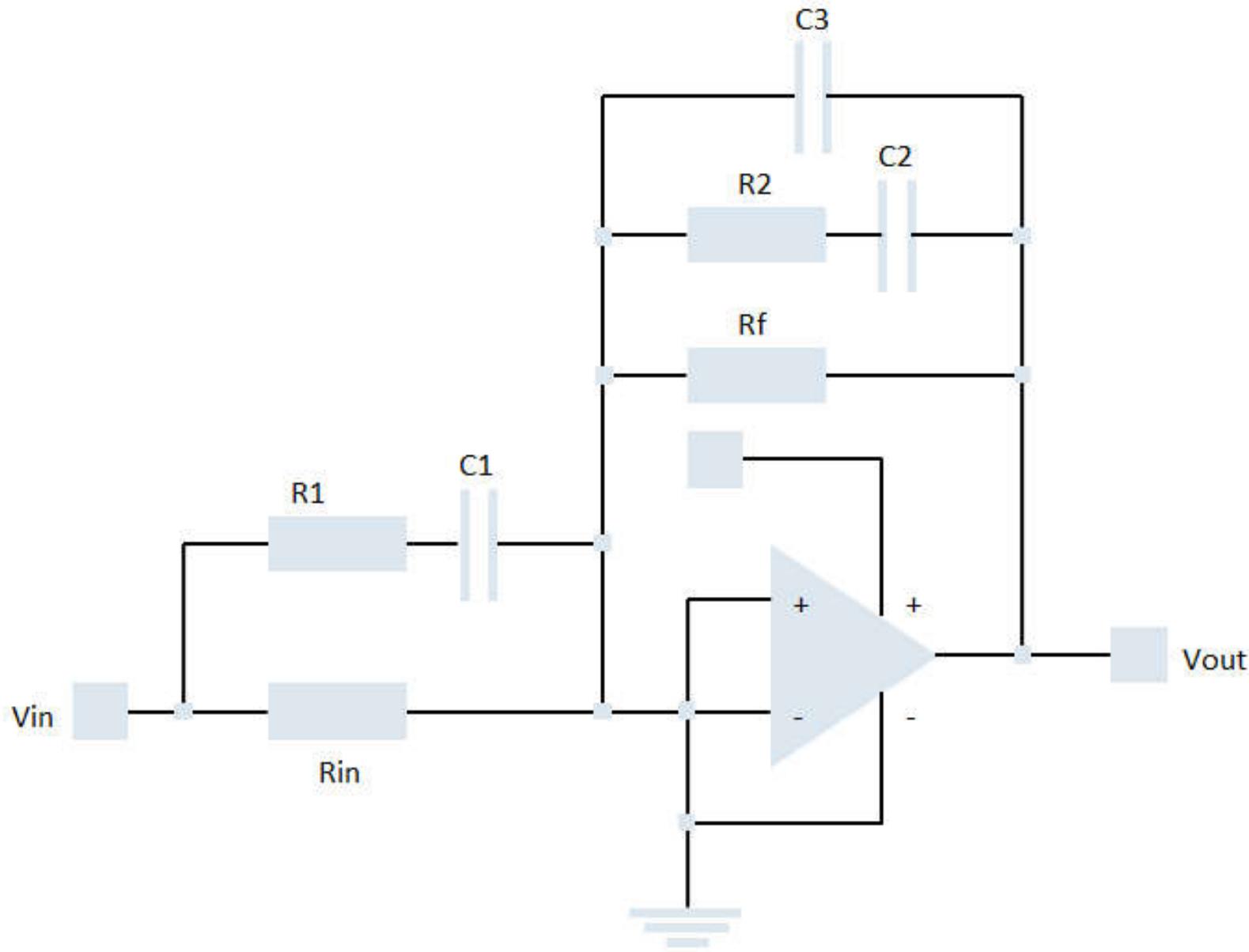


Amplifier Gain

▼ Introduction

In this application, we will plot the gain of the following amplifier circuit, for both the ideal and non-ideal response



> restart:

```
with(DynamicSystems):  
with(plots):
```

▼ Parameters

```
>  $R_1 := 1000$ :  
 $C_1 := 10^{-7}$ :  
 $R_{in} := 1000$ :  
 $C_3 := 4.7 \cdot 10^{-8}$ :  
 $R_2 := 1000$ :  
 $C_2 := 4.70 \cdot 10^{-7}$ :
```

$$R_f := 10^{102} :$$

Amplifier bandwidth factors

$$> \text{GBP} := 10^6 :$$

$$> \text{LPF} := 300 :$$

▼ Support Function

$$> \text{II} := (Z1, Z2) \rightarrow \frac{Z1 \cdot Z2}{Z1 + Z2} :$$

▼ Transfer functions

$$> Z_1 := R_1 + \frac{1}{s \cdot C_1} :$$

$$> Z_2 := R_2 + \frac{1}{s \cdot C_2} :$$

$$> Z_{ln} := \text{II}(R_{ln}, Z_1) :$$

$$> \text{factor}(Z_{ln})$$

$$\frac{500 (s + 10000)}{s + 5000} \quad (4.1)$$

$$> Z_{fb} := \text{II}\left(R_f, \text{II}\left(Z_2, \frac{1}{s \cdot C_3}\right)\right) :$$

Ideal Amplifier Gain

$$> G_{EAideal} := \text{factor}\left(\frac{Z_{fb}}{Z_{ln}}\right)$$

$$G_{EAideal} := \frac{42553.19148 (s + 2127.659574) (s + 5000.)}{(s + 1.93423597710^{-96}) (s + 23404.25531) (s + 10000.)} \quad (4.2)$$

Nonideal Op-Amp effects: Finite open loop gain

$$> \beta := \frac{1}{1 + G_{EAideal}} :$$

Finite open loop gain

$$> A_{vo} := \frac{\text{GBP}}{\text{LPF}} \cdot \frac{1}{\left(1 + \frac{s}{2 \cdot \pi \cdot \text{LPF}}\right) \cdot \left(1 + \frac{s}{2 \cdot \pi \cdot \text{GBP}}\right)}$$

$$A_{vo} := \frac{10000}{3 \left(1 + \frac{1}{600} \frac{s}{\pi}\right) \left(1 + \frac{1}{2000000} \frac{s}{\pi}\right)} \quad (4.3)$$

$$> \text{simplify}((4.3), \text{'size'})$$

$$\frac{400000000000000 \pi^2}{(600 \pi + s) (2000000 \pi + s)} \quad (4.4)$$

Nonideal error amplifier gain

$$\begin{aligned} > G_{EA} := \text{simplify}\left(G_{EAideal} \cdot \frac{1}{1 + \frac{1}{A_{vo} \cdot \beta}}\right) \\ G_{EA} := & (42553.19148(s + 5000)(s + 2127.659574)) / (1.012406241s^3 + 33512.60113s^2 + 2.342758273 \cdot 10^8 s \\ & + 1.358080578 \cdot 10^8 + 1.611267141 \cdot 10^{-7}s^4 + 2.53302959 \cdot 10^{-14}s^5) \end{aligned} \quad (4.5)$$

▼ Analysis

```
> with(DynamicSystems) :  
> sys1 := TransferFunction(G_{EA}) :  
> sys2 := TransferFunction(G_{EAideal}) :  
> p1 := PhasePlot(sys1, range = 10 .. 100000, hertz = true, legend = "Non-ideal") :  
> p2 := PhasePlot(sys2, range = 10 .. 100000, hertz = true, legend = "Ideal", color = black) :  
> display(p1, p2)
```

